
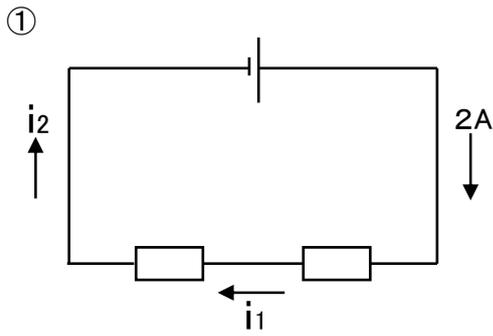


【電流】




年 番 名 前

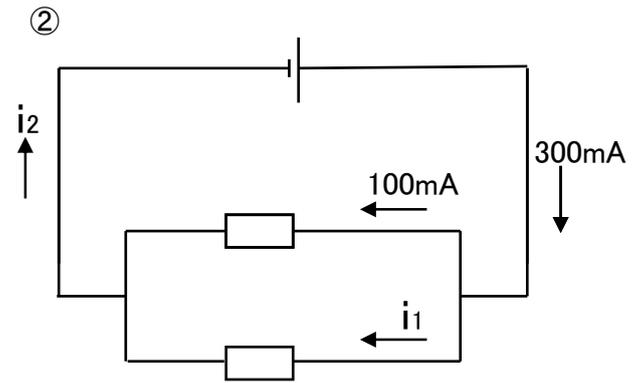


$i_1 = \underline{\hspace{2cm}}$ $i_2 = \underline{\hspace{2cm}}$




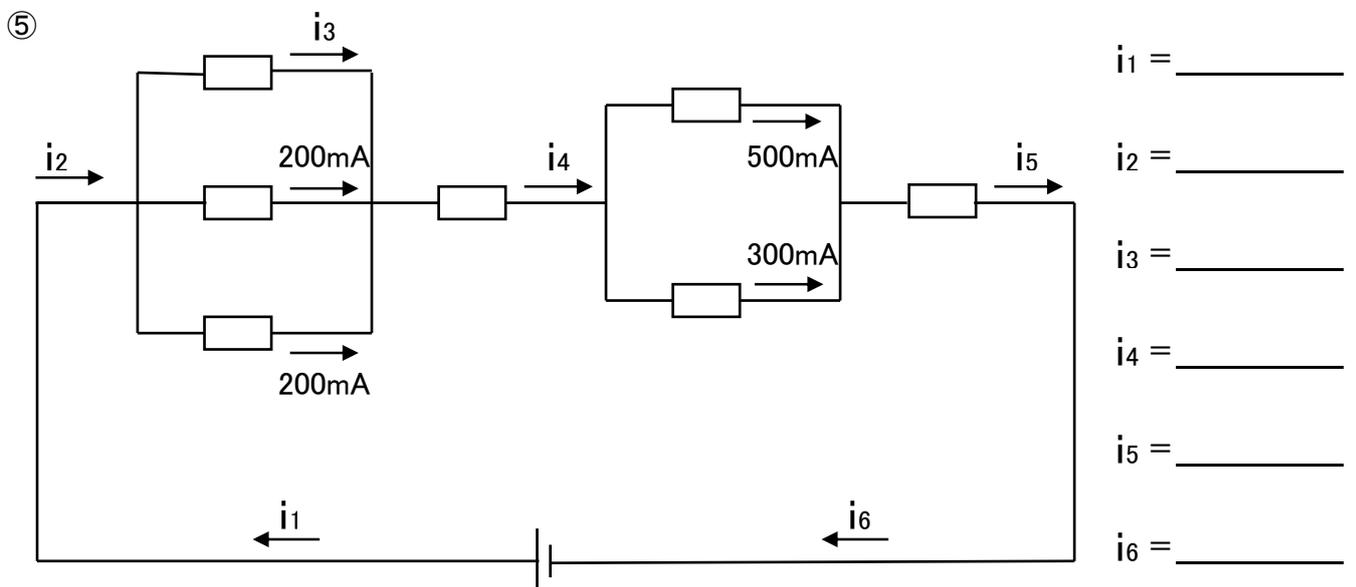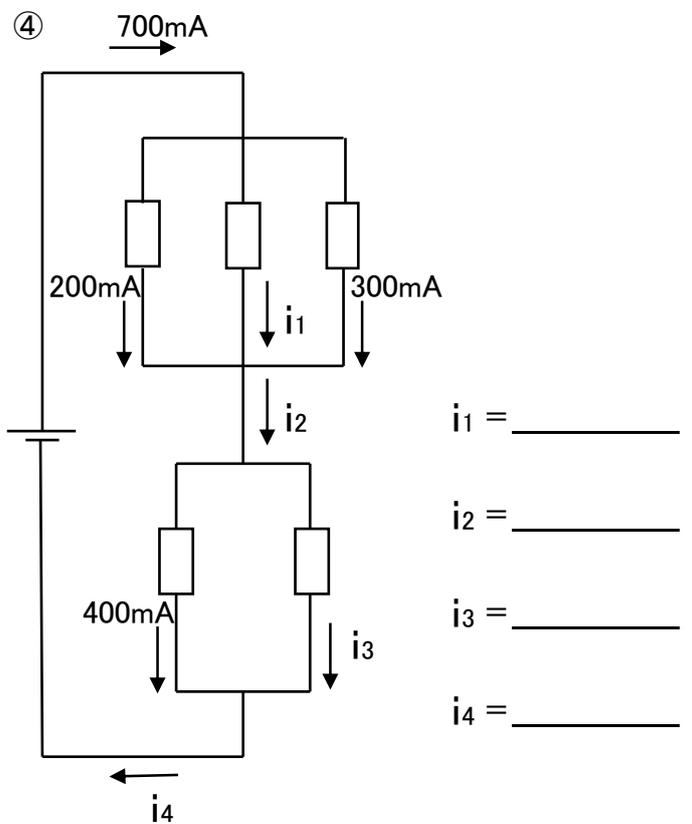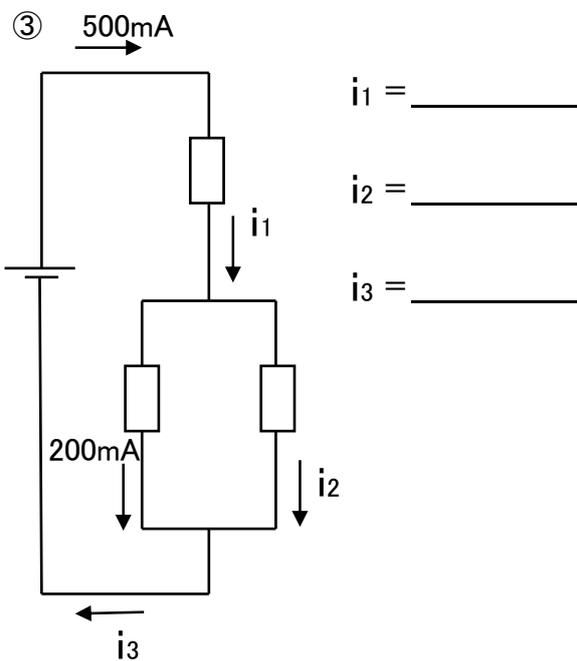$i_1 = \underline{\hspace{2cm}}$ $i_2 = \underline{\hspace{2cm}}$




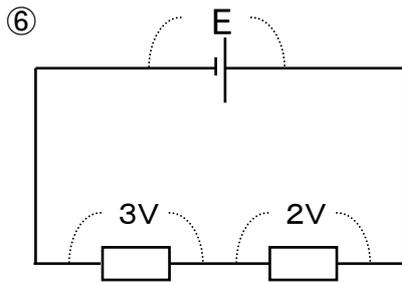


$E = \underline{\hspace{2cm}}$

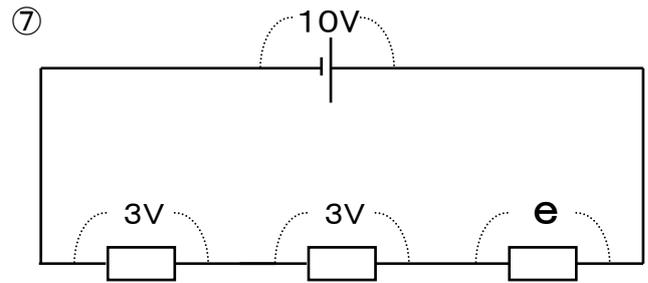




$e = \underline{\hspace{2cm}}$

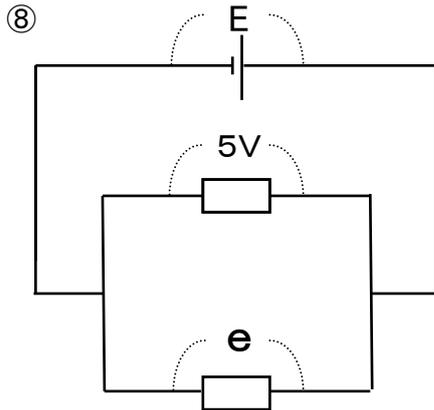

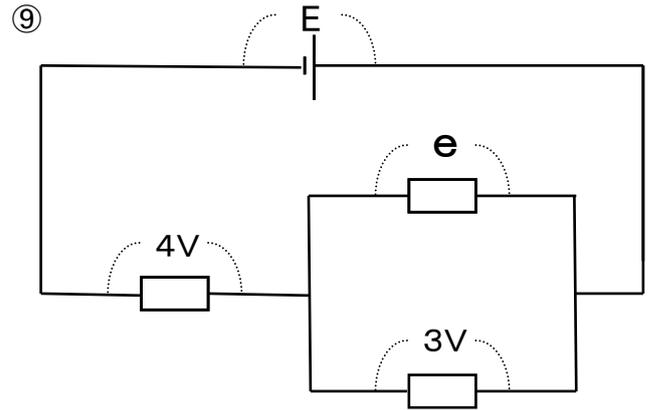$e = \underline{\hspace{2cm}}$ $E = \underline{\hspace{2cm}}$



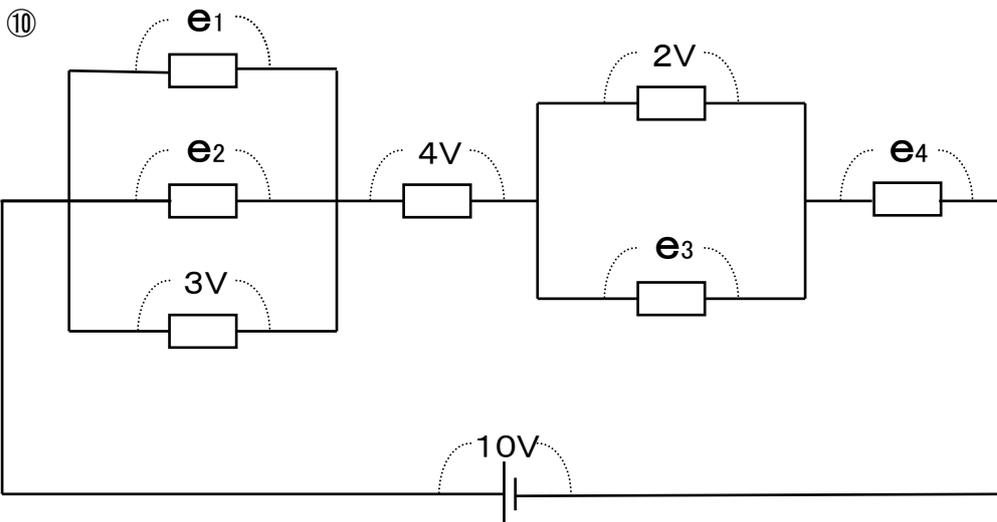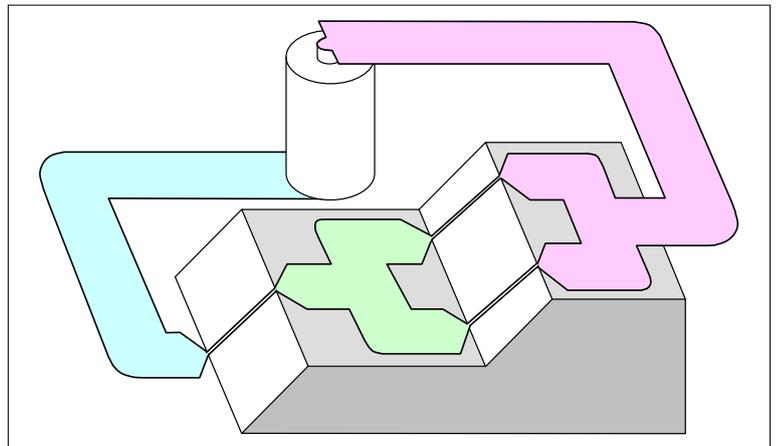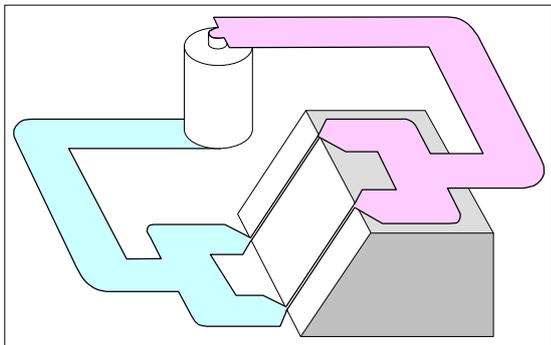$e = \underline{\hspace{2cm}}$ $E = \underline{\hspace{2cm}}$



$e_1 = \underline{\hspace{2cm}}$

$e_2 = \underline{\hspace{2cm}}$

$e_3 = \underline{\hspace{2cm}}$

$e_4 = \underline{\hspace{2cm}}$