

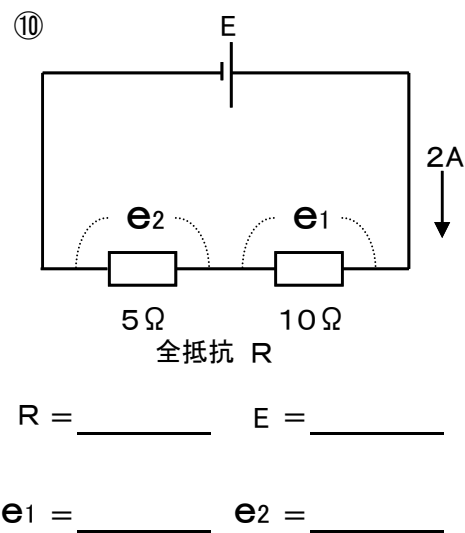
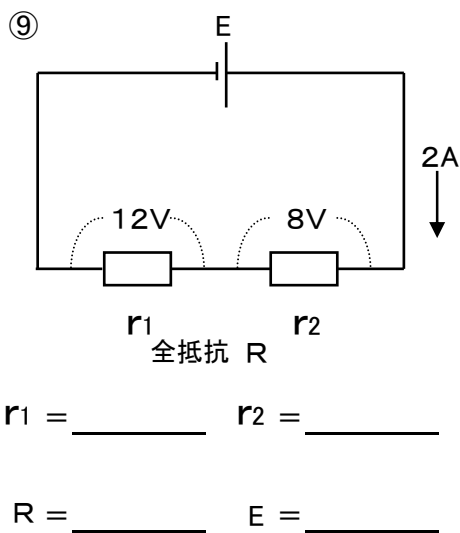
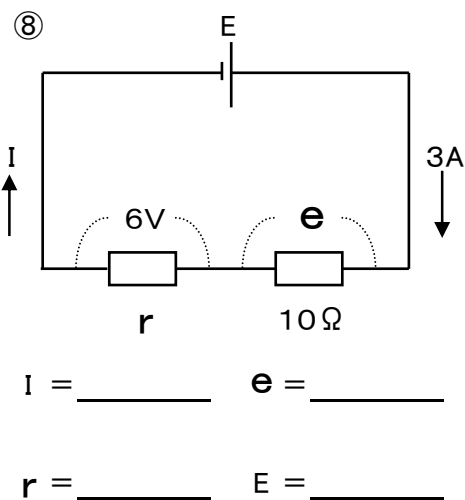
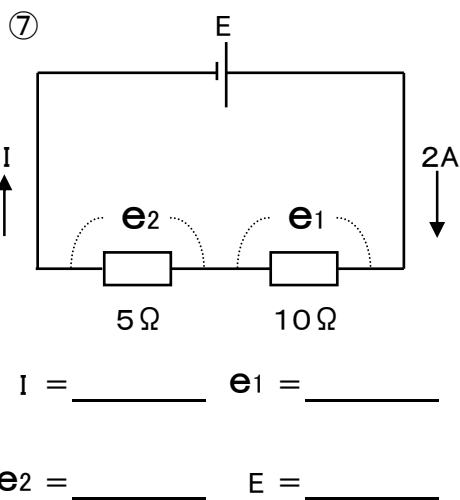
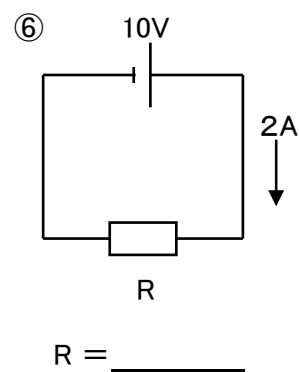
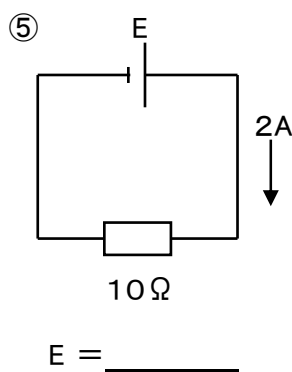
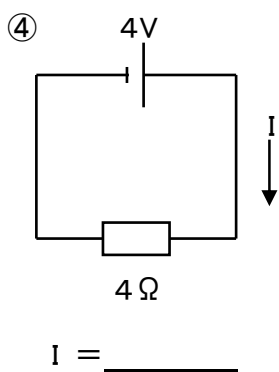
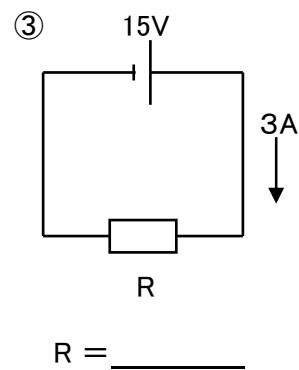
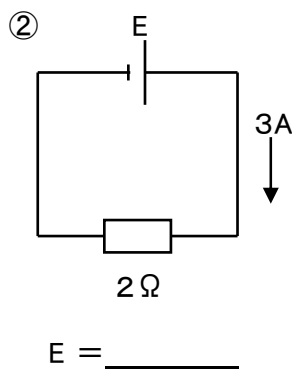
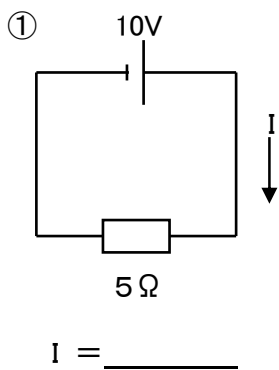
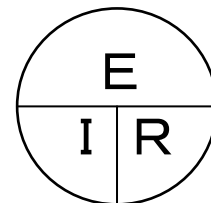


オームの法則練習問題


年 番 名前 _____

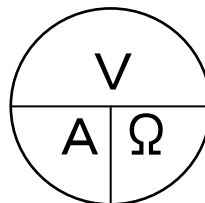

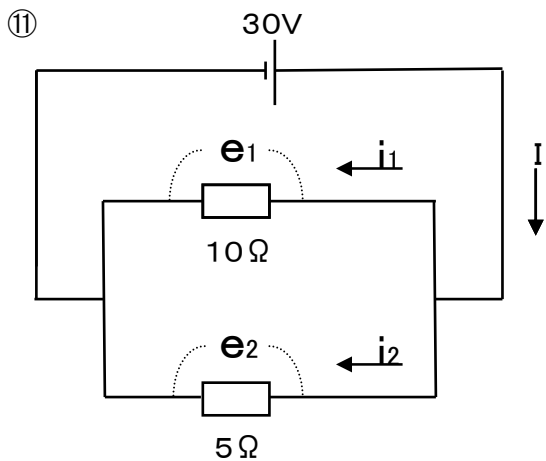


$e_1 = \underline{\hspace{2cm}}$ $e_2 = \underline{\hspace{2cm}}$

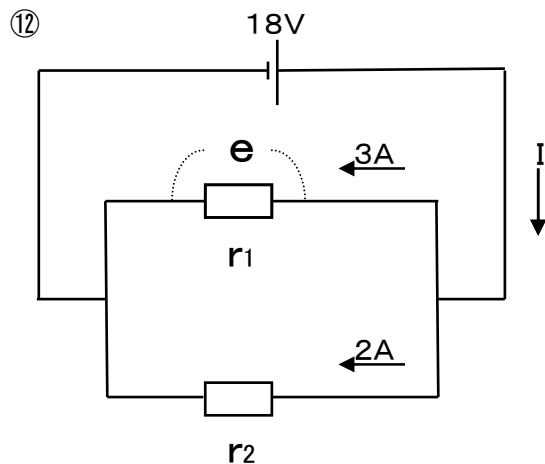$i_1 = \underline{\hspace{2cm}}$ $i_2 = \underline{\hspace{2cm}}$ $I = \underline{\hspace{2cm}}$




$e = \underline{\hspace{2cm}}$ $r_1 = \underline{\hspace{2cm}}$

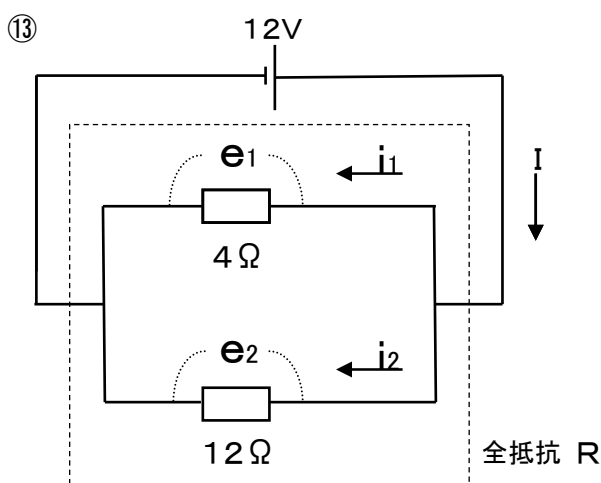$r_2 = \underline{\hspace{2cm}}$ $I = \underline{\hspace{2cm}}$




$e_1 = \underline{\hspace{2cm}}$ $e_2 = \underline{\hspace{2cm}}$ $i_1 = \underline{\hspace{2cm}}$

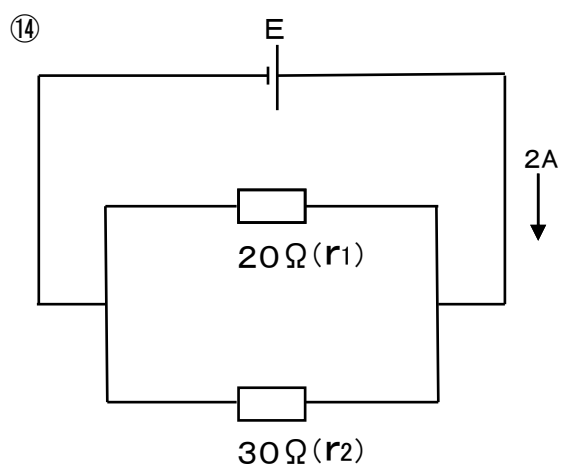$i_2 = \underline{\hspace{2cm}}$ $I = \underline{\hspace{2cm}}$ $R = \underline{\hspace{2cm}}$



全抵抗 $R = \frac{r_1 \times r_2}{r_1 + r_2} = \frac{\quad \times \quad}{\quad + \quad}$
 $= \underline{\hspace{2cm}} = \underline{\hspace{2cm}}$

$E = \underline{\hspace{2cm}}$

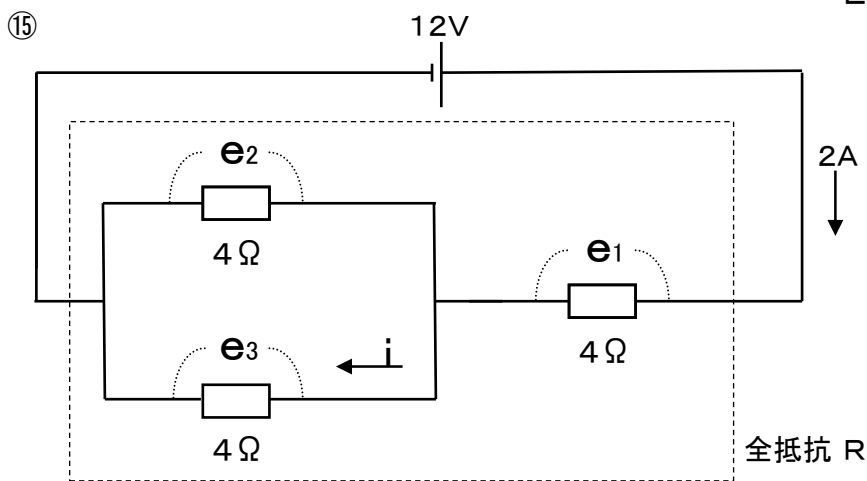

$e_1 = \underline{\hspace{2cm}}$ $e_2 = \underline{\hspace{2cm}}$ $e_3 = \underline{\hspace{2cm}}$

$i = \underline{\hspace{2cm}}$ 全抵抗 $R = \underline{\hspace{2cm}}$

